

1 | Capacitors

- Batteries try to push electrons in a direction.
 - Zooming in on each end, would one see some charge since the electrons within the positive terminal would leave
 - * Yes, but tiny (this is tiny capacitance)
- Capacitors are designed to store amounts of charge in compact volumes
 - Two conducting plates that connect to batteries and the high surface area allows significant amount of charge (one negative plate, one pos)
 - Net charge of a capacitor is zero due to cancellation. Charge usually refers to positive plate in this context.
- No current flows across a capacitor as there is a gap of air/plastic (insulator called dielectric) between them.
 - This insulator is to prevent loss of all charge as they would cancel when given the opportunity to touch
- Capacitors have no cap when it comes to storing things (think water balloon vs bucket) and it varies related to voltage.
- At same voltage, capacitors can vary in stored charge because of differences in area and distance between plates (and quality of dielectric)

$$C = \frac{Q}{V} \text{ in units of } \frac{\text{Coulombs}}{\text{Volts}} \text{ or } \frac{\text{Coulombs}^2}{\text{Joules}}$$

$$C = k\epsilon_0 \frac{A}{d} \text{ where } A \text{ is plate area and } d \text{ plate separation. } \epsilon_0 \text{ shows up in Coulomb's Law as well.}$$

- Dielectric will polarize due to attempted transfer of electrons
- Capacitors are one-way (sort of like LEDs), and the shorter end is negative

2 | Batteries vs. Capacitors

Batteries convert stored chemical potential energy into electrical energy. Capacitors store electrical potential energy and converting it to electrical energy,

Batteries maintain constant voltages as charge flow out (until it exhausts chemicals). Capacitors decrease linearly in voltage as charge flows out (charge remaining is capacitance times voltage).

Energy stored in capacitors can be calculated through looking at the units. $E = \frac{V_c \cdot Q}{2} \text{ Joules} = \frac{\frac{\text{Joules}}{\text{Coulomb}} \cdot \text{Coulomb}}{2}$ 1/2 comes from the average voltage (also can be thought of integral of voltage over charge flowed out) $E = \frac{V_c \cdot Q}{2} = \frac{CV^2}{2}$ is energy stored on a charged capacitor (second equation derived from use of $Q = CV$)

2.1 | Water analogy

Capacitors are like a flexible membrane stretched across a pipe. Applying pressure will have it flex and eventually this will hit a maximum and stop (pressures reach equilibrium). The volume of water in the membrane is proportional to the pressure, much like how $Q \propto V$. Bigger capacitors are larger more flexible membranes, and vice versa.

3 | Charging Time

Experimental evidence suggests $\tau = RC$. *Unit check!* $R = \frac{\text{Volts} \cdot \text{Seconds}}{\text{Coulombs}}$ and $C = \frac{\text{Coulombs}}{\text{Volt}}$ so $RC = \text{Seconds}$

4 | Derivations

Assume battery of voltage V_b , resistor of resistance R , and capacitor of capacitance C . Assume measurement of current I is possible (note that there is a switch in the circuit). I will be a function of *time*.

$$I(t) = \frac{V_b}{R} e^{-\frac{t}{RC}} \quad V_c(t) = V_b(1 - e^{-\frac{t}{RC}})$$